

## PIC LCD frequency counter

This project is just a pcb for a variant of the “Weeder Frequency Counter” published at: <http://www.piclist.com/techref/piclist/weedfreq.htm>


On that web site is a link to a modified version of the ASM software by Barry Smith: <http://www.piclist.com/techref/piclist/weedfreq/4bitlcdusart.htm>

Barry's software version allows either a PIC16f84 or a PIC16f628 to be used with the LCD in 4 bit mode, which simplifies the pcb layout slightly and provides the option of a serial data output if using the 16f628 chip.

As there is no link to a circuit or pcb layout for Barry's version, I have made my own pcb as shown here.

It is a single sided board with 4 jumper wire links and is small enough to fit behind the lcd module if you use the same type as mine. (single row connector at top of the module)  
I did not bother with any preamp transistors as I will only be using it to show the frequency of my old valve-based Heathkit model AO-1U Sine-Square audio generator.

## Circuit

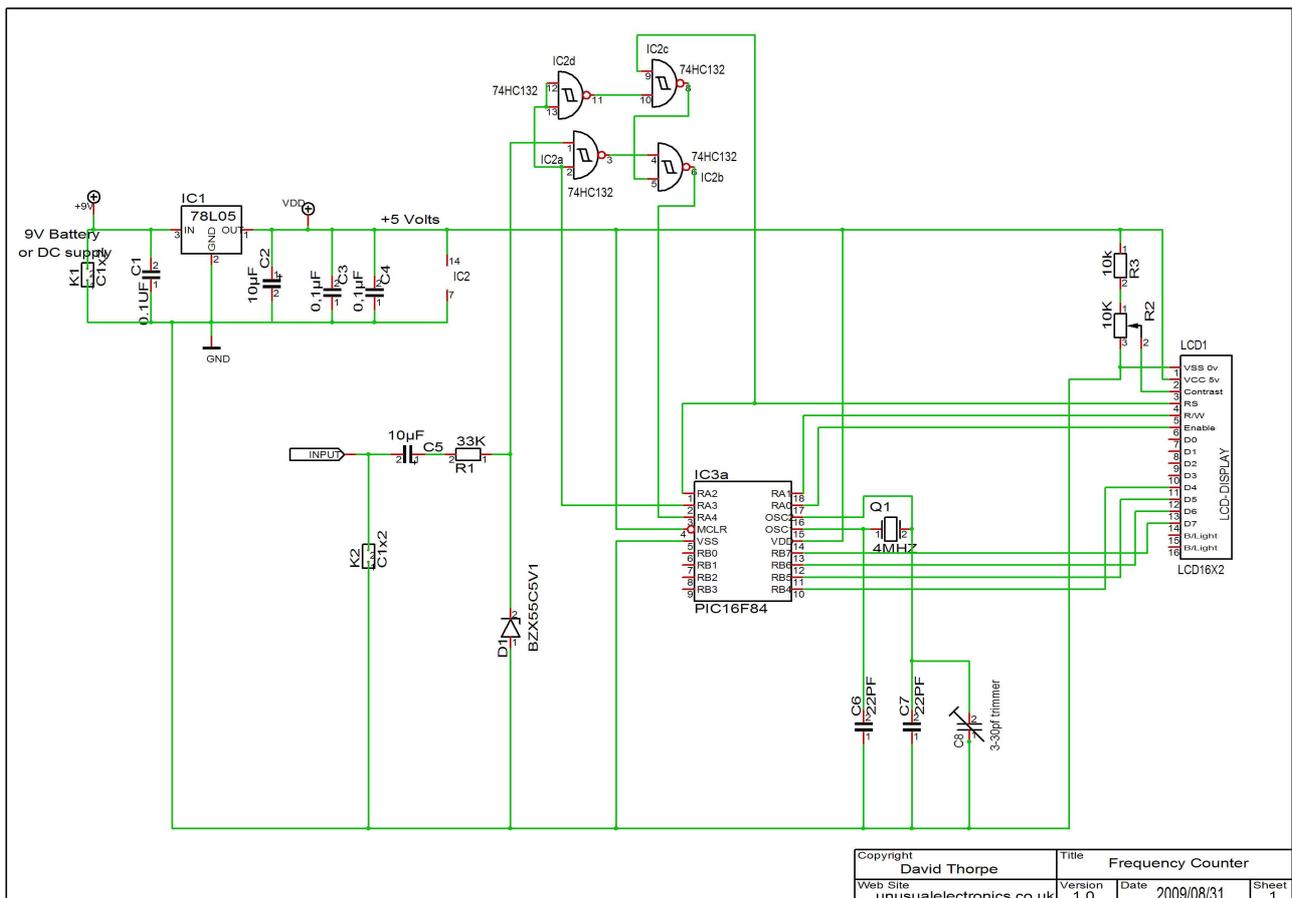


Reduce value of C7 to 10pF if using Trimmer (C8)

I used a 16x2 line LCD module (although only a 16x1 line type is needed)

A PIC16F628 can be substituted for the 16F84 if you wish.

## Board layout

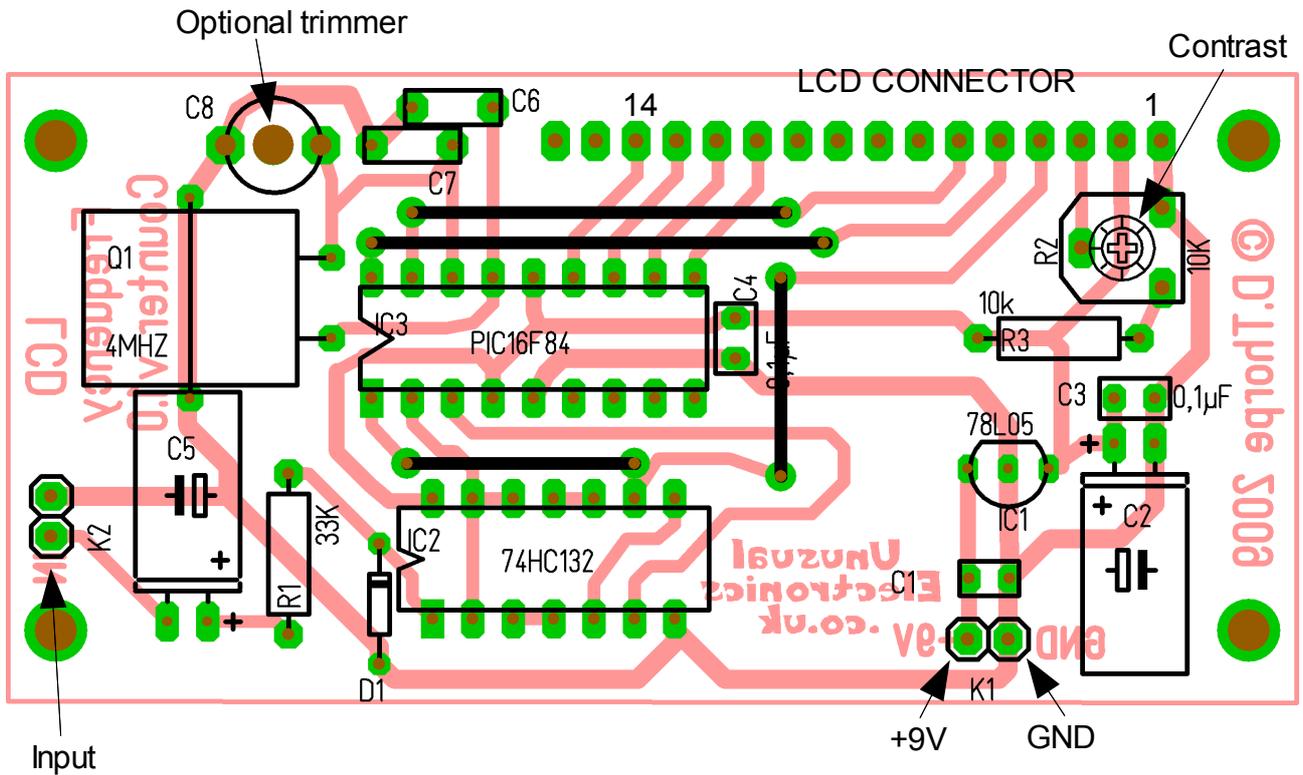

The pcb is slightly larger than an lcd module, which can be attached directly to the under-side of the board if it's pinout is in exactly the same position as mine.

C8 is a calibration trimmer capacitor if you need better accuracy. You may have to reduce the value of C7 if you use it.


Power consumption is about 6mA (with no lcd backlight), it can be powered from a 9 volt battery.

## PCB Track Layout

The circuit can be built on this single sided pcb layout.

PCB is shown actual size: 81 x 39.77 mm and is ready for printing, using the toner transfer method.

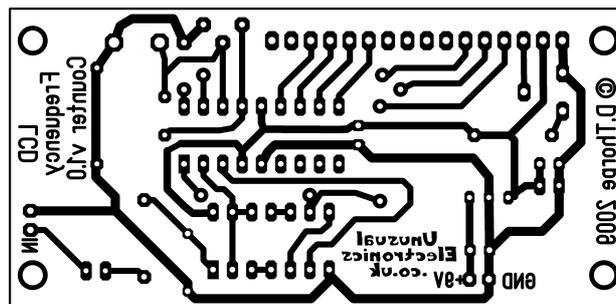Print this page actual size (ensure that print option for "Page Scaling" is set to "None")



## **Disclaimer**

This project is provided on an "AS-IS" basis WITHOUT WARRANTY of any kind, either express or implied. I shall NOT BE LIABLE in any way to you or to any other person, firm or corporation whatsoever for any loss, liability, damage (whether direct or consequential), personal injury or expense of any nature whatsoever arising from inaccuracies, errors in, or the use or inability to use the hardware and/or software here.

D. Thorpe ([www.unusualelectronics.co.uk](http://www.unusualelectronics.co.uk))